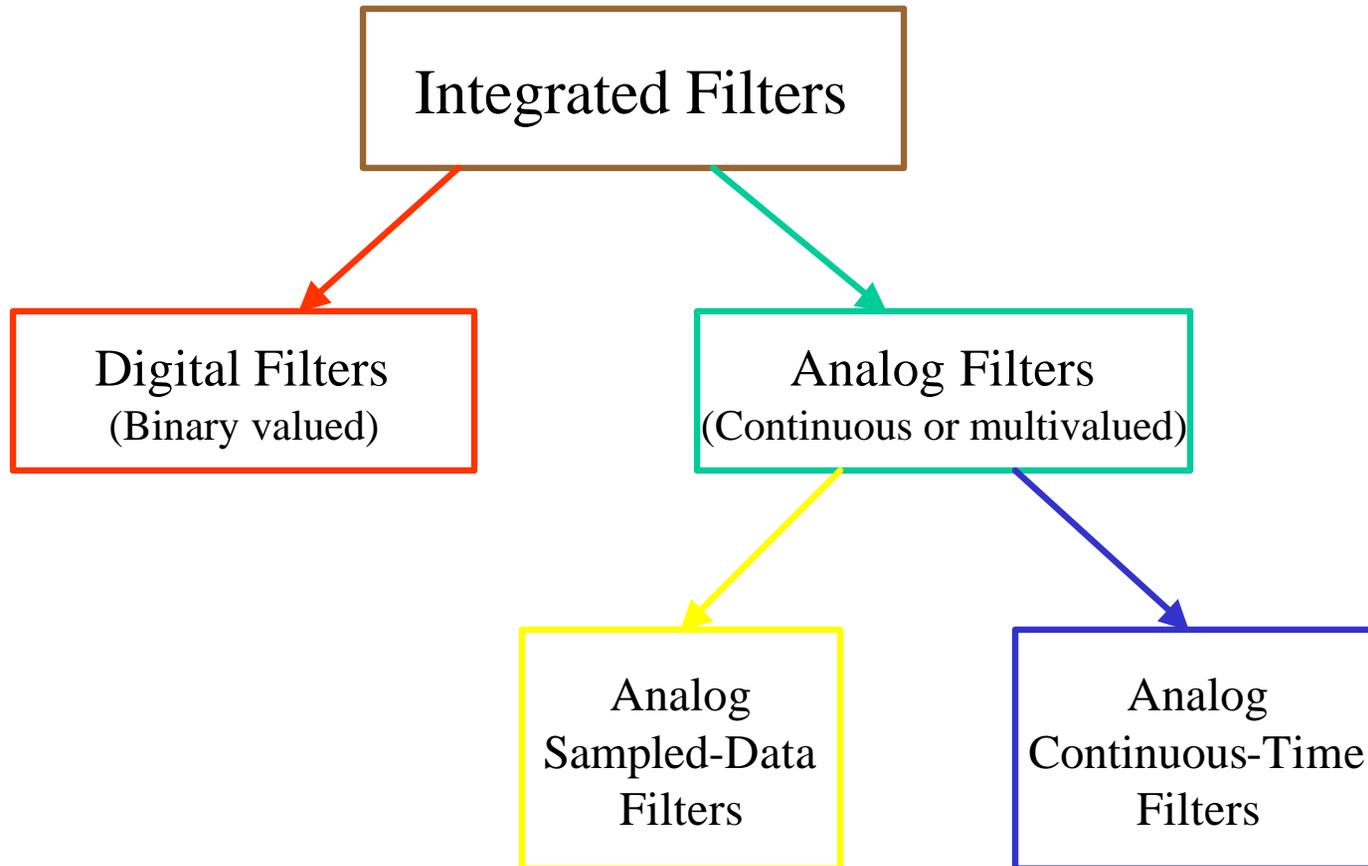



# Signal Processing Design of Integrated Analog and Digital Filters

Prof. Paul Hasler

# Types of Integrated Filters




# Where to divide Analog and Digital?

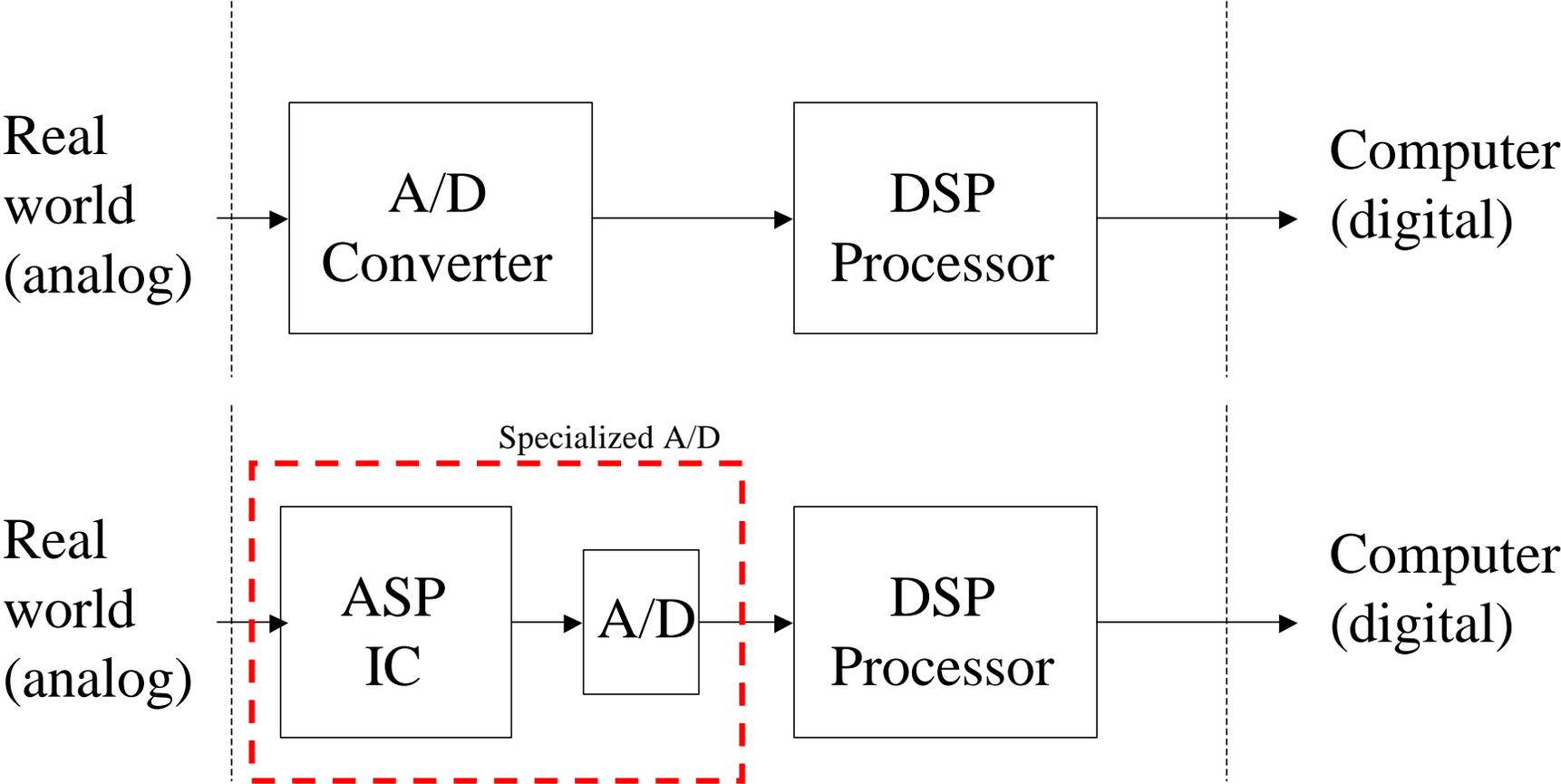

# Analog-Digital Comparison

Low SNR: Analog / High SNR: Digital

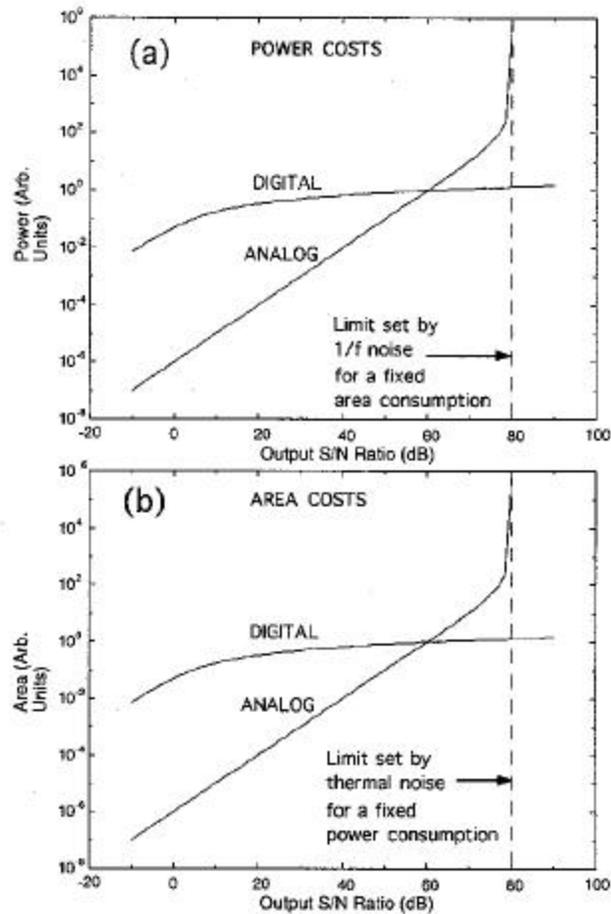


[Sarpekar 1997]


# Analog-Digital Comparison

Low SNR: Analog / High SNR: Digital

Practical Interpretation of Cost

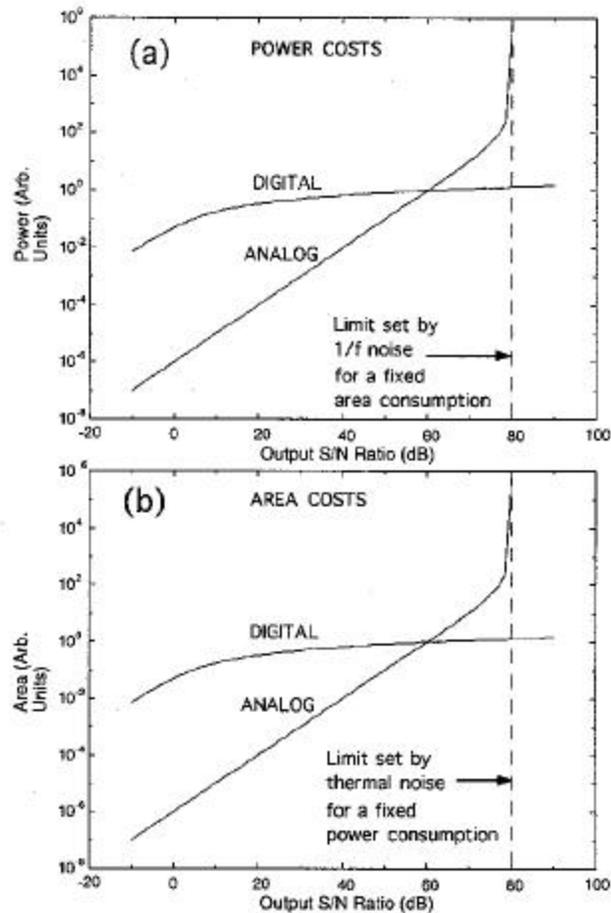

[Sarpekar 1997]

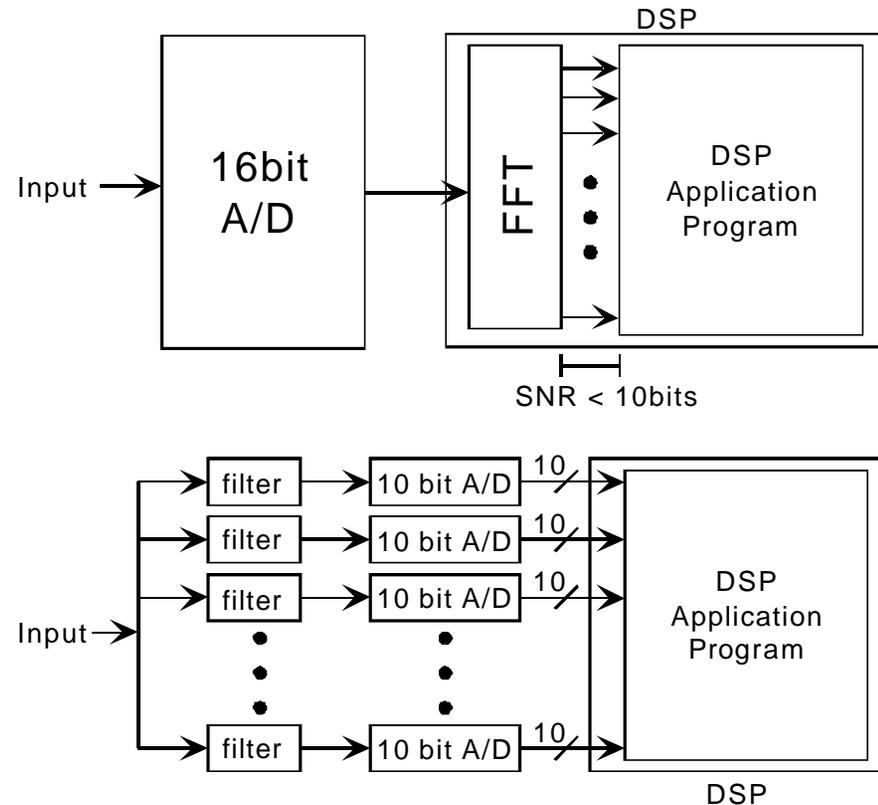

- What if exponentially spaced FFT?

# Circuit Issues for Filters

Programmability / Tunability: flexibility and complexity

Available for digital (clocks/ crystals) as well as  
some analog (e.g. Floating-Gate) filters

# Circuit Issues for Filters

Programmability / Tunability: flexibility and complexity

Available for digital (clocks/ crystals) as well as  
some analog (e.g. Floating-Gate) filters

High Signal-to-Noise Ratio (resolution):

Ratio of the largest signal and the smallest signal

**Largest signal:** Harmonic Distortion (continuous-time filters), Range limitations

**Smallest Signal:** Noise

# Circuit Issues for Filters

**Programmability / Tunability: flexibility and complexity**

Available for digital (clocks/ crystals) as well as  
some analog (e.g. Floating-Gate) filters

**High Signal-to-Noise Ratio (resolution):**

Ratio of the largest signal and the smallest signal

**Largest signal:** Harmonic Distortion (continuous-time filters), Range limitations

**Smallest Signal:** Noise

**Insensitivity to environmental fluctuations:**

**Power-supply:** Power Supply Rejection Ratio (**PSRR**)

Temperature, etc.



Not a problem for digital filters,  
but can be the cause of several  
problems to other analog circuits

# Circuit Issues for Filters

**Programmability / Tunability: flexibility and complexity**

Available for digital (clocks/ crystals) as well as  
some analog (e.g. Floating-Gate) filters

**High Signal-to-Noise Ratio (resolution):**

Ratio of the largest signal and the smallest signal

**Largest signal:** Harmonic Distortion (continuous-time filters), Range limitations

**Smallest Signal:** Noise

**Insensitivity to environmental fluctuations:**

**Power-supply:** Power Supply Rejection Ratio (**PSRR**)

**Temperature, etc.**



Not a problem for digital filters,  
but can be the cause of several  
problems to other analog circuits

Typically, sampling in amplitude / time results in,


- the more complexity is needed ( S/H blocks, anti-aliasing filters),
- more power / lower-frequency / area

# Design of Analog Filters

- Find the transfer function for a given filter
- “Partition” the transfer function, or an approximation, into simple parts that can be implemented.
- Implement the transfer function in a particular circuit technology
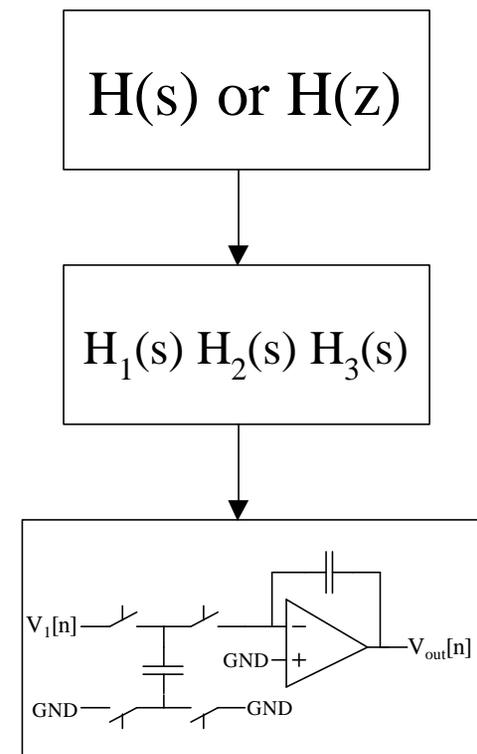
# Design of Analog Filters

- Find the transfer function for a given filter
- “Partition” the transfer function, or an approximation, into simple parts that can be implemented.
- Implement the transfer function in a particular circuit technology




# Design of Analog Filters


As basic building blocks we have

- integrators, delay elements
- first-order (low-pass / bandpass)
- second order functions  
(low-pass / bandpass / highpass)

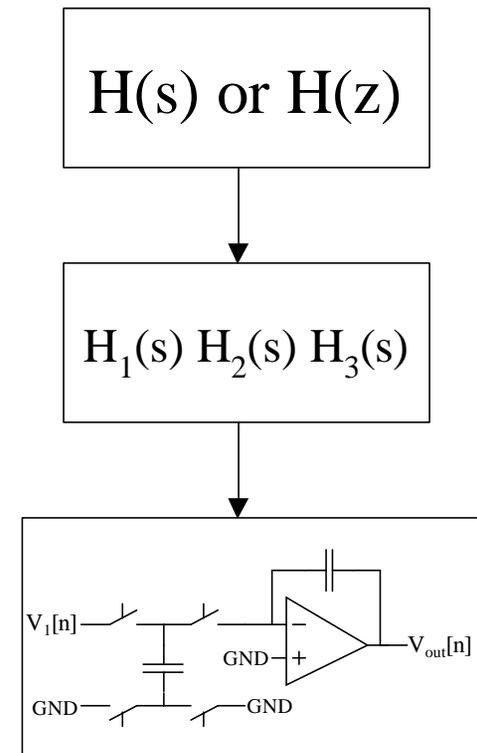
The “circuit” design question is  
how to make these functions  
what inputs / outputs / internal variables  
should be voltages / currents, etc.




# Design of Analog Filters

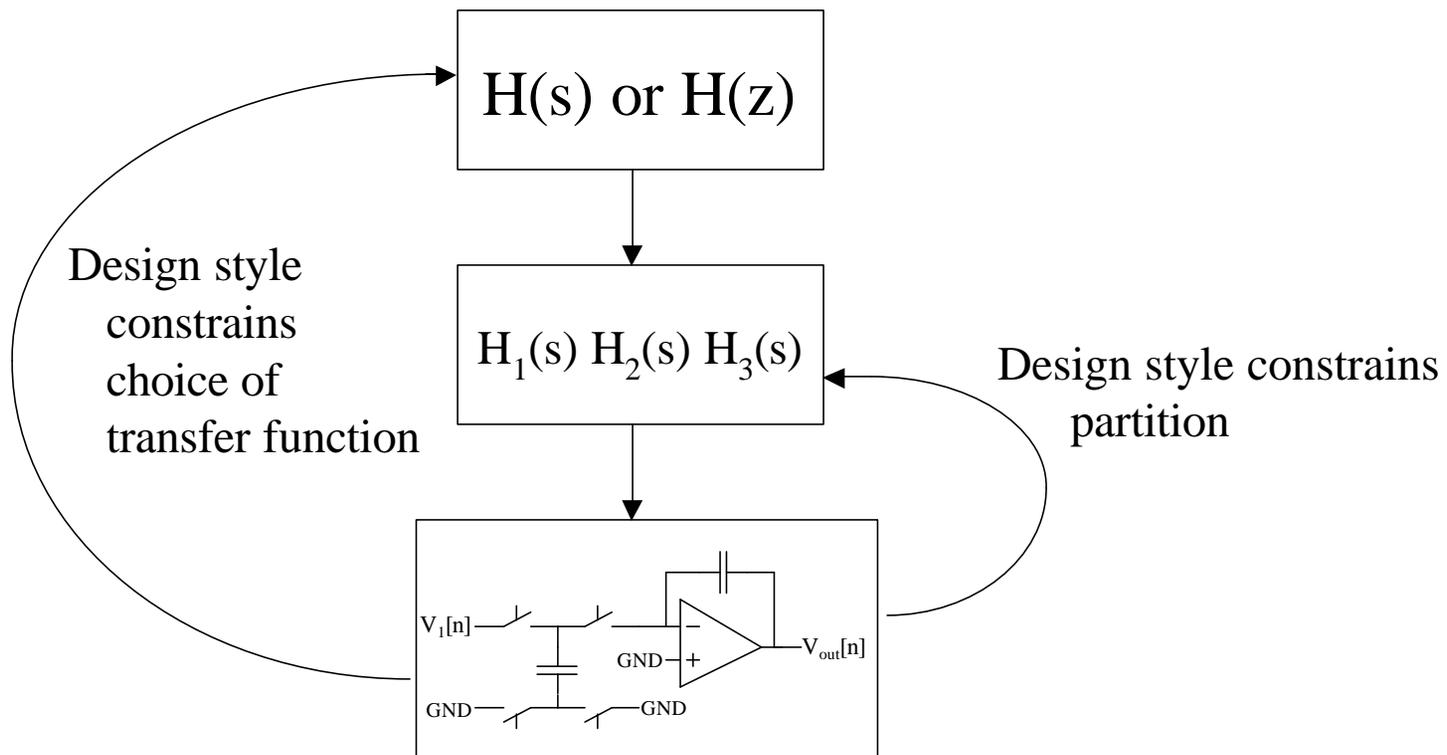


# Choosing $H(s)$ or $H(z)$ for a filter

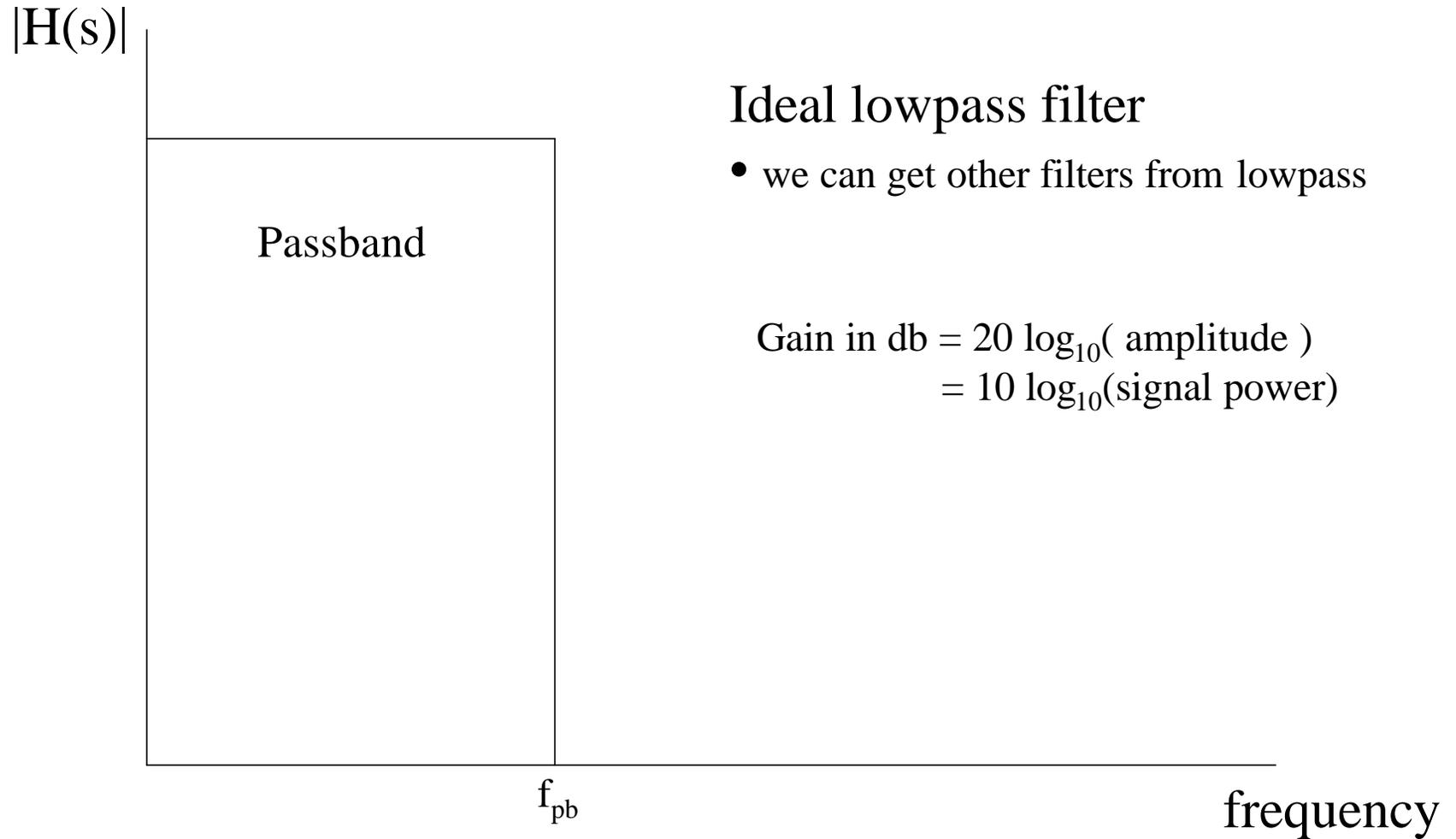


# H(s) or H(z) for a lowpass filter

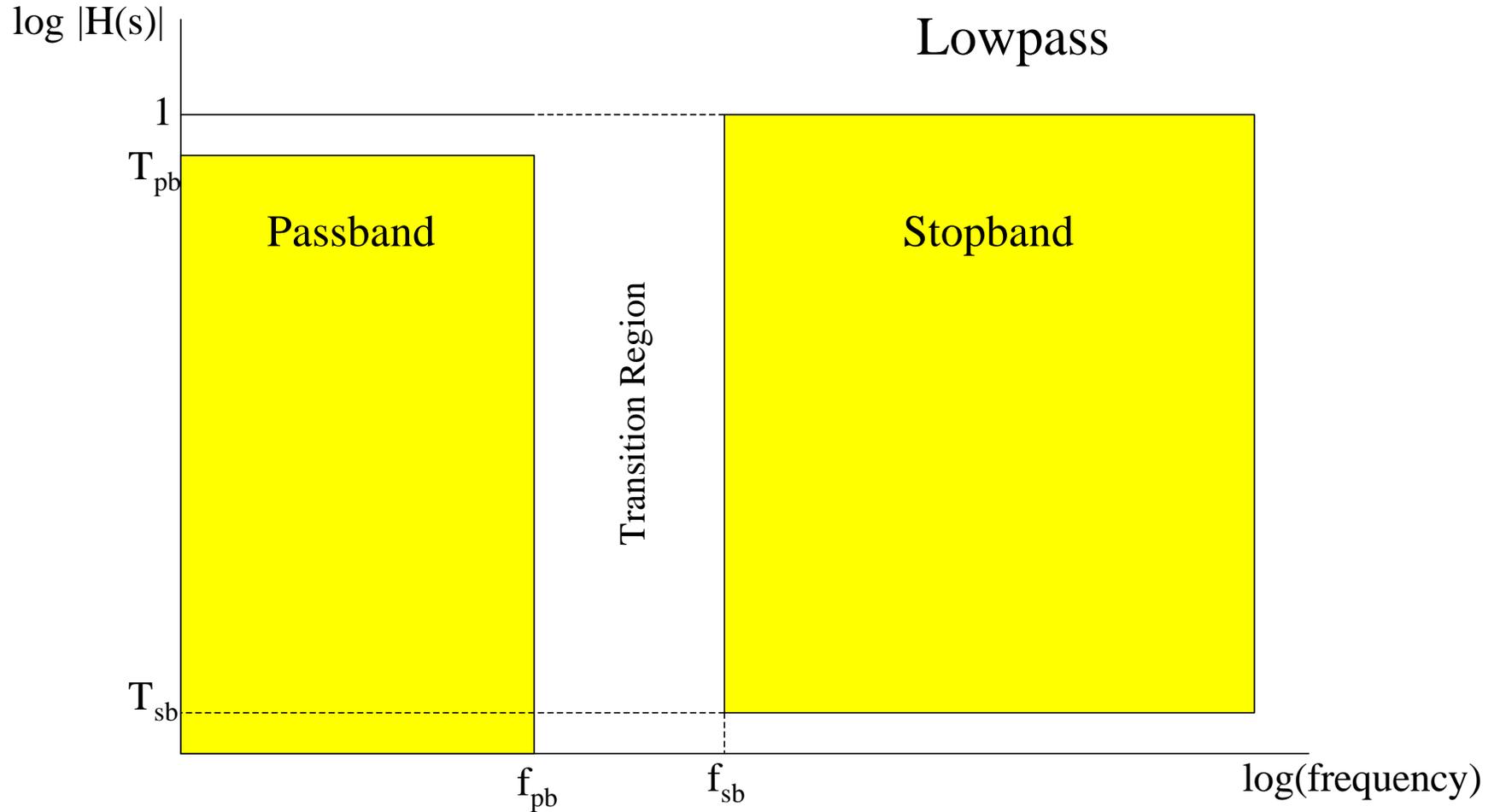


# H(s) or H(z) for a lowpass filter

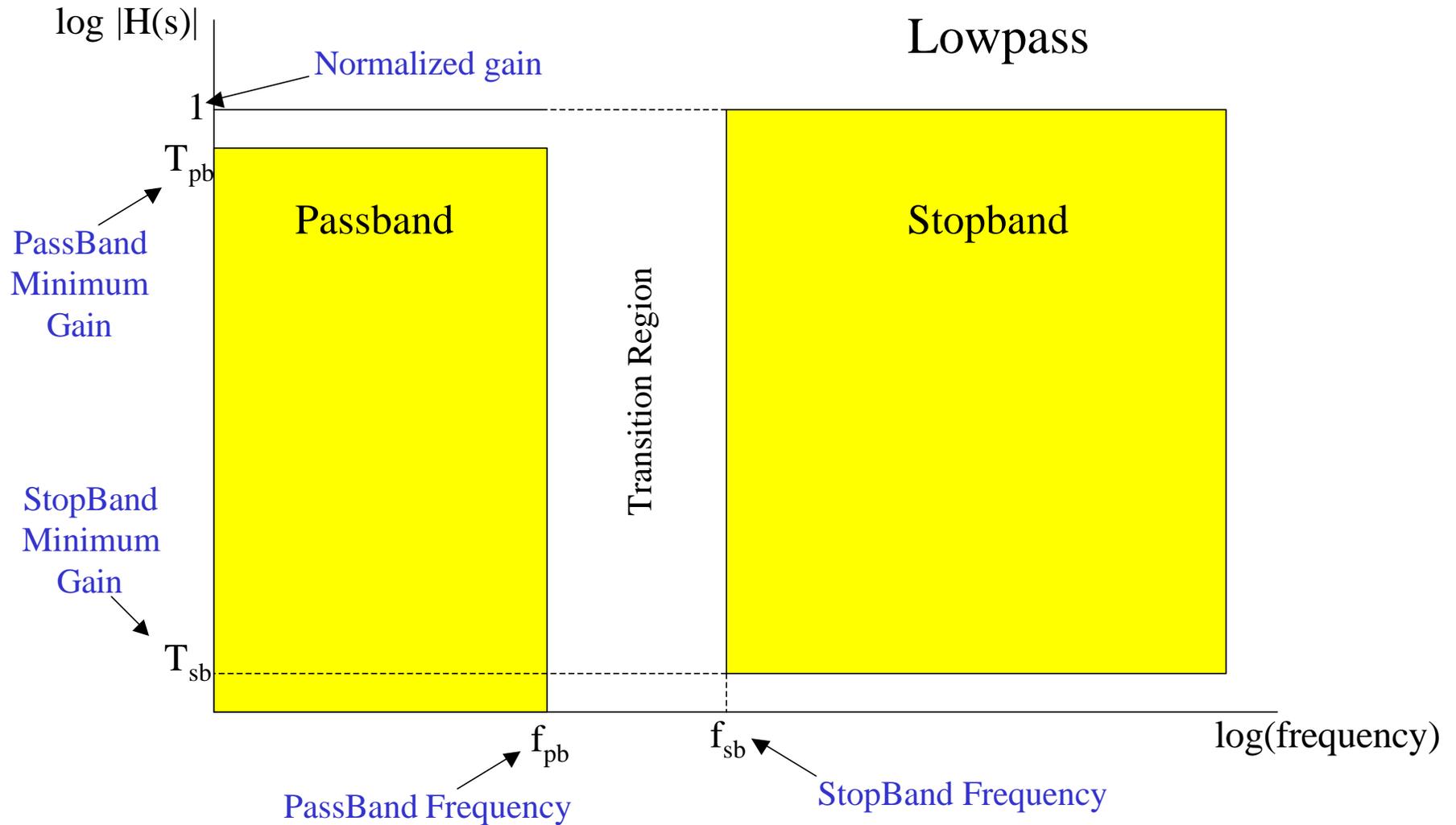

# H(s) or H(z) for a Highpass filter

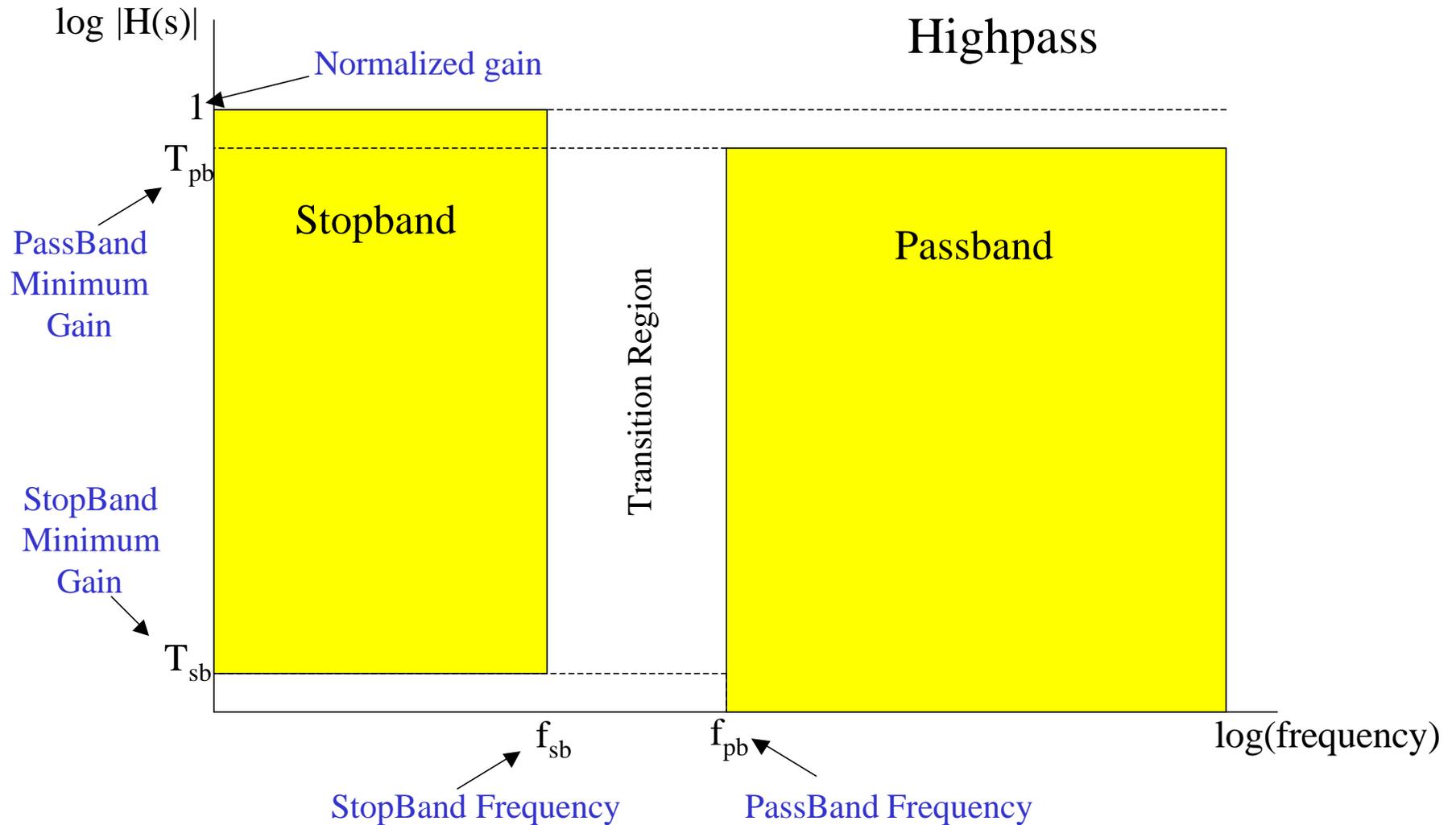

# H(s) or H(z) for a Highpass filter

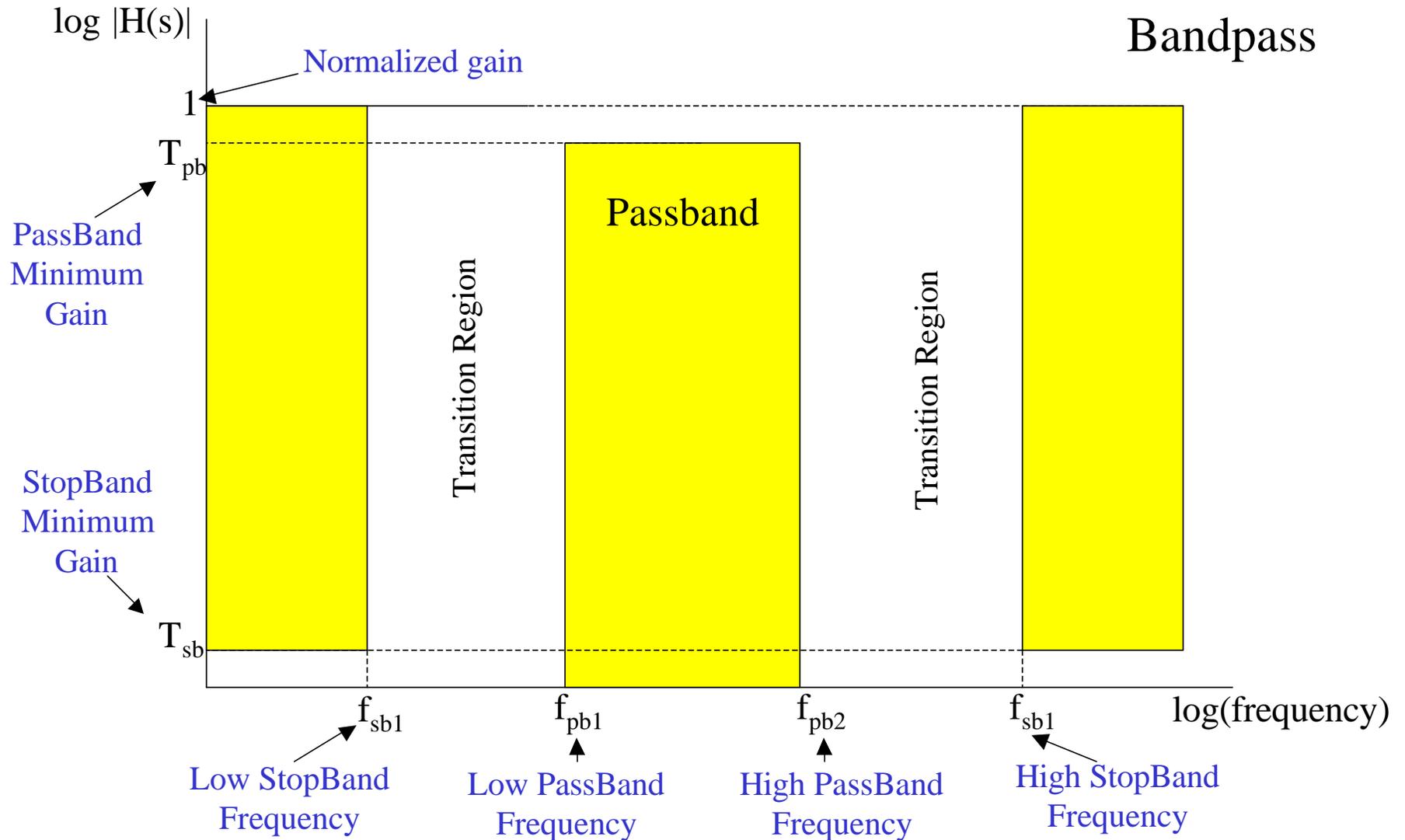

# Four Canonical Cont-Time Filters

## Classic Analog Filters (IIR digital filters):

Butterworth: Maximally flat in passband...moderate rolloff

Chebyshev : Faster rolloff by allowing ripples in passband or stopband

Elliptic: Fastest rolloff by allowing ripples in both passband and stopband

Bessel: Near linear phase, slow rolloff

# Four Canonical Cont-Time Filters

## Classic Analog Filters (IIR digital filters):

Butterworth: Maximally flat in passband...moderate rolloff

Chebyshev : Faster rolloff by allowing ripples in passband or stopband

Elliptic: Fastest rolloff by allowing ripples in both passband and stopband

Bessel: Near linear phase, slow rolloff

Other FIR (digital) filters....

Other filter design ( $H(s)$  or  $H(z)$ ) techniques: Optimization approaches

Should we choose  $H(s)$  or  $H(z)$  for our representation?

Partially due to particular circuit tradeoffs

(tunability? tools? continuous tunability? Accuracy? power consumption?)

What happens if we just cascade first order stages?


$$T(s) = \frac{1}{(1 + j s\tau)^N}$$

# What happens if we just cascade first order stages?

$$T(s) = \frac{1}{(1 + js\tau)^N}$$

Corner shifts with N

Rolloff is not initially sharp.....

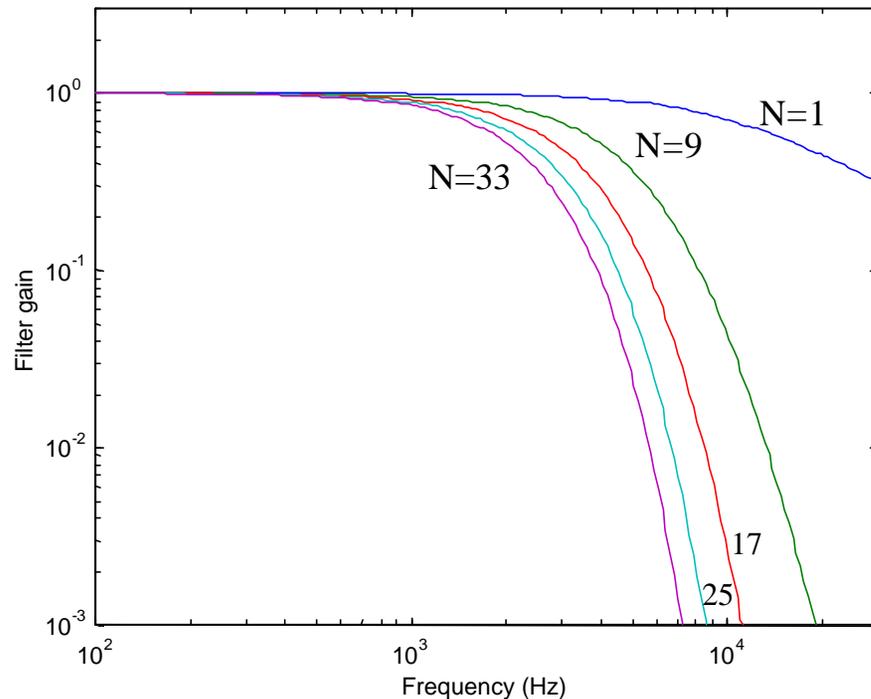

# Butterworth Filter Design

## Transfer Function: (low-pass)

$$T(s) = \frac{1}{1 + (-1)^{N+1} \varepsilon s^N \tau^N}$$

$$|T(j\omega)| = \frac{1}{\sqrt{1 + \varepsilon^2 \omega^{2N} \tau^{2N}}}$$

## Definition of $\varepsilon$ :

$$T_{pb} = \frac{1}{\sqrt{1 + \varepsilon^2}} \quad (f_{sb} \tau = 2\pi)$$

$$T_{pb} = 1/\sqrt{2} \text{ for } \varepsilon = 1$$

# Butterworth Filter Design

## Transfer Function: (low-pass)

$$T(s) = \frac{1}{1 + j(-1)^{N+1} \varepsilon^2 s^N \tau^N}$$

$$|T(j\omega)| = \frac{1}{\sqrt{1 + \varepsilon^2 \omega^{2N} \tau^{2N}}}$$

## Definition of $\varepsilon$ :

$$T_{pb} = \frac{1}{\sqrt{1 + \varepsilon^2}} \quad (f_{pb} \tau = 2\pi)$$

$$T_{pb} = 1/\sqrt{2} \text{ for } \varepsilon = 1$$

Need to solve to meet the specification of  $T_{sb}$  at  $f_{sb}$  : Filter Order (N)

$$T_{sb}^2 \left( 1 + \varepsilon^2 (f_{sb} / f_{pb})^{2N} \right) = 1$$

To meet specifications, one chooses the next largest integer

# Butterworth Filter Design

## Transfer Function: (low-pass)

$$T(s) = \frac{1}{1 + j(-1)^{N+1} \varepsilon^2 s^N \tau^N}$$

$$|T(j\omega)| = \frac{1}{\sqrt{1 + \varepsilon^2 \omega^{2N} \tau^{2N}}}$$

## Definition of $\varepsilon$ :

$$T_{pb} = \frac{1}{\sqrt{1 + \varepsilon^2}} \quad (f_{sb} \tau = 2\pi)$$

$$T_{pb} = 1/\sqrt{2} \text{ for } \varepsilon = 1$$

Need to solve to meet the specification of  $T_{sb}$  at  $f_{sb}$  : Filter Order (N)

$$T_{sb}^2 ( 1 + \varepsilon^2 (f_{sb} / f_{pb})^{2N} ) = 1$$



To meet specifications, one chooses the next largest integer

## Pole locations: ( $\varepsilon = 1$ )

$$1/\tau_k = (1/\tau) (\sin( (2k-1)\pi/(2N) ) + j \cos( (2k-1)\pi/(2N) ) ), \quad k=1\dots N$$

$$T(j\omega) = \frac{1}{(1 + s \tau_1) (1 + s \tau_2) \dots (1 + s \tau_N)}$$

# Butterworth Filter Design

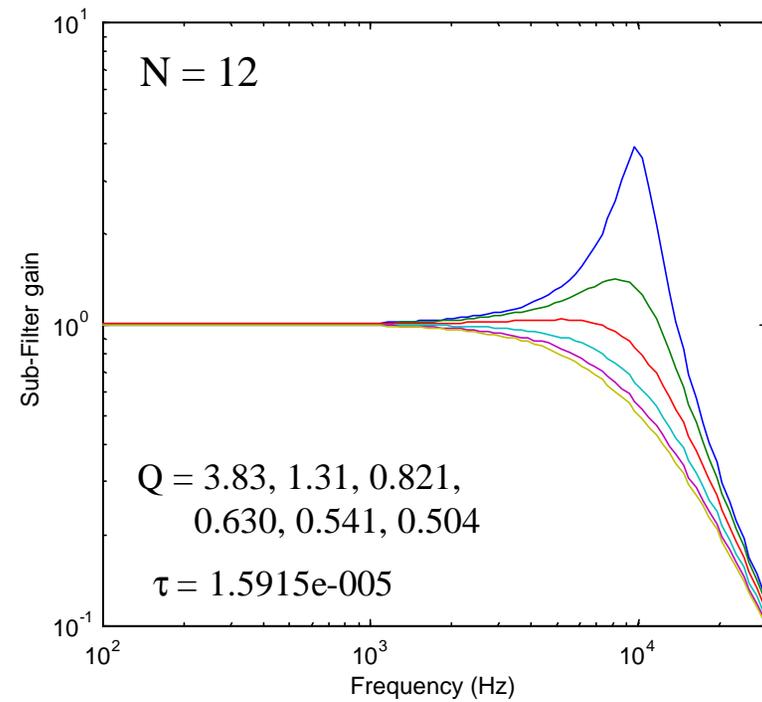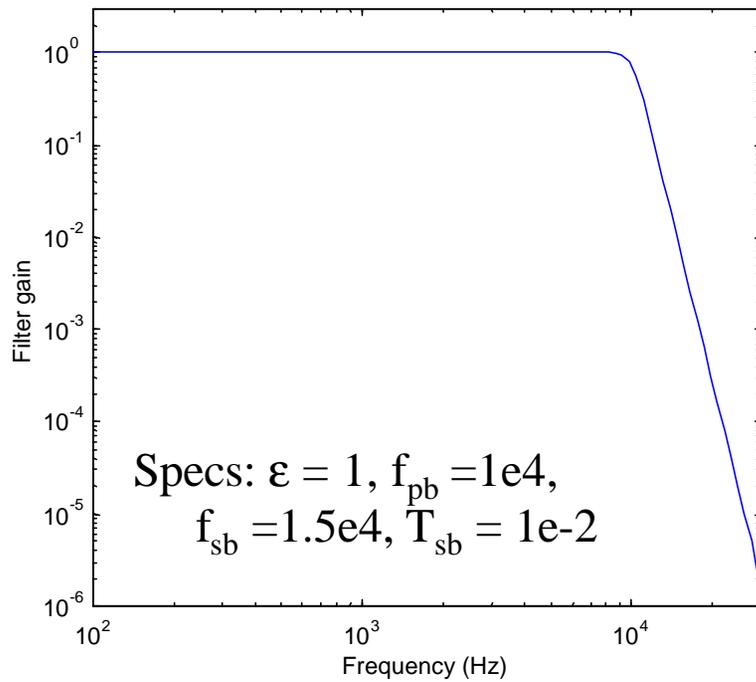

# Chebyshev Filter Design

## Transfer Function(low-pass)

$$|T(j\omega)| = \frac{1}{\sqrt{1 + \varepsilon^2 \cos^2(N \cos^{-1}(\omega\tau))}} \quad \omega\tau > 1$$
$$= \frac{1}{\sqrt{1 + \varepsilon^2 \cosh^2(N \cosh^{-1}(\omega\tau))}} \quad \omega\tau < 1$$

## Definition of $\varepsilon$ :

$$T_{pb} = \frac{1}{\sqrt{1 + \varepsilon^2}}$$

( $f_{pb} \tau = 2\pi$ )

$$T_{pb} = 1/\sqrt{2} \text{ for } \varepsilon = 1$$

# Chebyshev Filter Design

## Transfer Function(low-pass)

$$|T(j\omega)| = \frac{1}{\sqrt{1 + \varepsilon^2 \cos^2(N \cos^{-1}(\omega\tau))}} \quad \omega\tau > 1$$

$$= \frac{1}{\sqrt{1 + \varepsilon^2 \cosh^2(N \cosh^{-1}(\omega\tau))}} \quad \omega\tau < 1$$

## Definition of $\varepsilon$ :

$$T_{pb} = \frac{1}{\sqrt{1 + \varepsilon^2}}$$

( $f_{sb} \tau = 2\pi$ )

$$T_{pb} = 1/\sqrt{2} \text{ for } \varepsilon = 1$$

Need to solve to meet the specification of  $T_{sb}$  at  $f_{sb}$  : Filter Order (N)

$$(1 + \varepsilon^2 \cosh^2(N \cosh^{-1}(f_{sb} / f_{pb}))) T_{sb} = 1$$

# Chebyshev Filter Design

## Transfer Function(low-pass)

$$|T(j\omega)| = \frac{1}{\sqrt{1 + \varepsilon^2 \cos^2(N \cos^{-1}(\omega\tau))}} \quad \omega\tau > 1$$

$$= \frac{1}{\sqrt{1 + \varepsilon^2 \cosh^2(N \cosh^{-1}(\omega\tau))}} \quad \omega\tau < 1$$

## Definition of $\varepsilon$ :

$$T_{pb} = \frac{1}{\sqrt{1 + \varepsilon^2}}$$

( $f_{sb} \tau = 2\pi$ )

$$T_{pb} = 1/\sqrt{2} \text{ for } \varepsilon = 1$$

Need to solve to meet the specification of  $T_{sb}$  at  $f_{sb}$  : Filter Order (N)



$$(1 + \varepsilon^2 \cosh^2(N \cosh^{-1}(f_{sb} / f_{pb}))) T_{sb}^2 = 1$$

## Pole locations:

$$1/\tau_k = (1/\tau) \left( \sin((2k-1)\pi/(2N)) \sinh((1/N) \sinh^{-1}(1/\varepsilon)) \right. \\ \left. + j \cos((2k-1)\pi/(2N)) \cosh((1/N) \sinh^{-1}(1/\varepsilon)) \right)$$

Where k goes from 1, 2, ..., N

# Chebyshev Filter Design

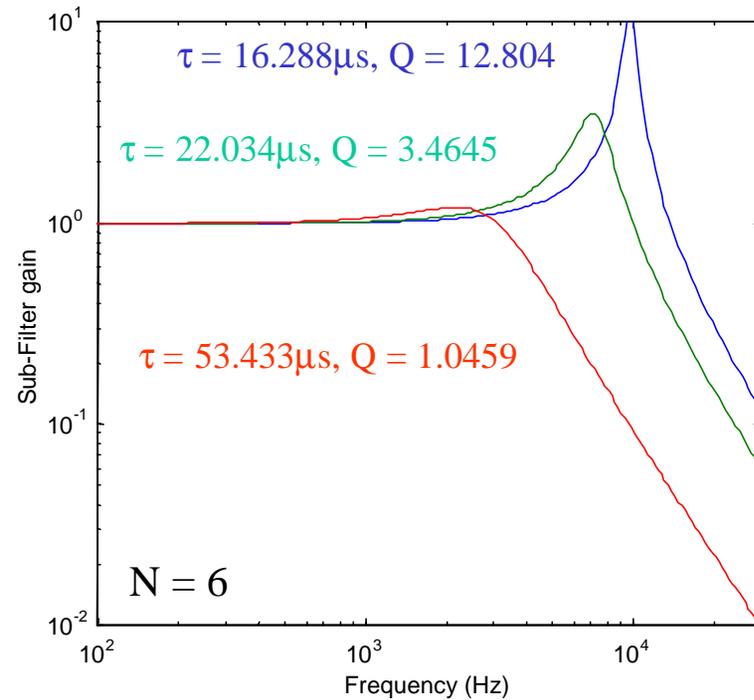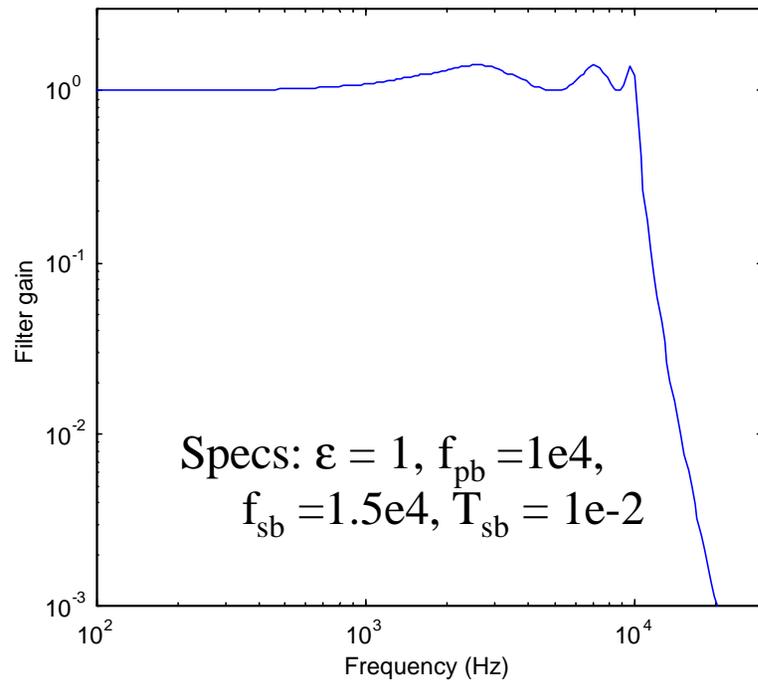

Fewer stages, higher Qs....

# Transformations between s and z

$$z^{-1} = e^{-sT}$$

T = sampling period

Simple Transformation

$$s \sim \frac{1}{T} (1 - z^{-1})$$

$$z^{-1} \sim 1 - sT$$

# Transformations between s and z

## Simple Transformation

$$z^{-1} = e^{-sT}$$

T = sampling period

$$s \sim \frac{1}{T} (1 - z^{-1})$$


$$z^{-1} \sim 1 - sT$$

## Bilinear transform

$$s \sim \frac{1}{T} \frac{1 - z^{-1}}{1 + z^{-1}} \sim \frac{1}{T} \frac{1 - e^{-sT}}{1 + e^{-sT}}$$

$$z^{-1} \sim \frac{1 - sT}{1 + sT} \sim \frac{1}{T} \frac{1 - (1 - sT + 0.5*(sT)^2 - \dots)}{1 + 1 - sT + 0.5*(sT)^2 - \dots} \sim s$$

# General Filter Topology

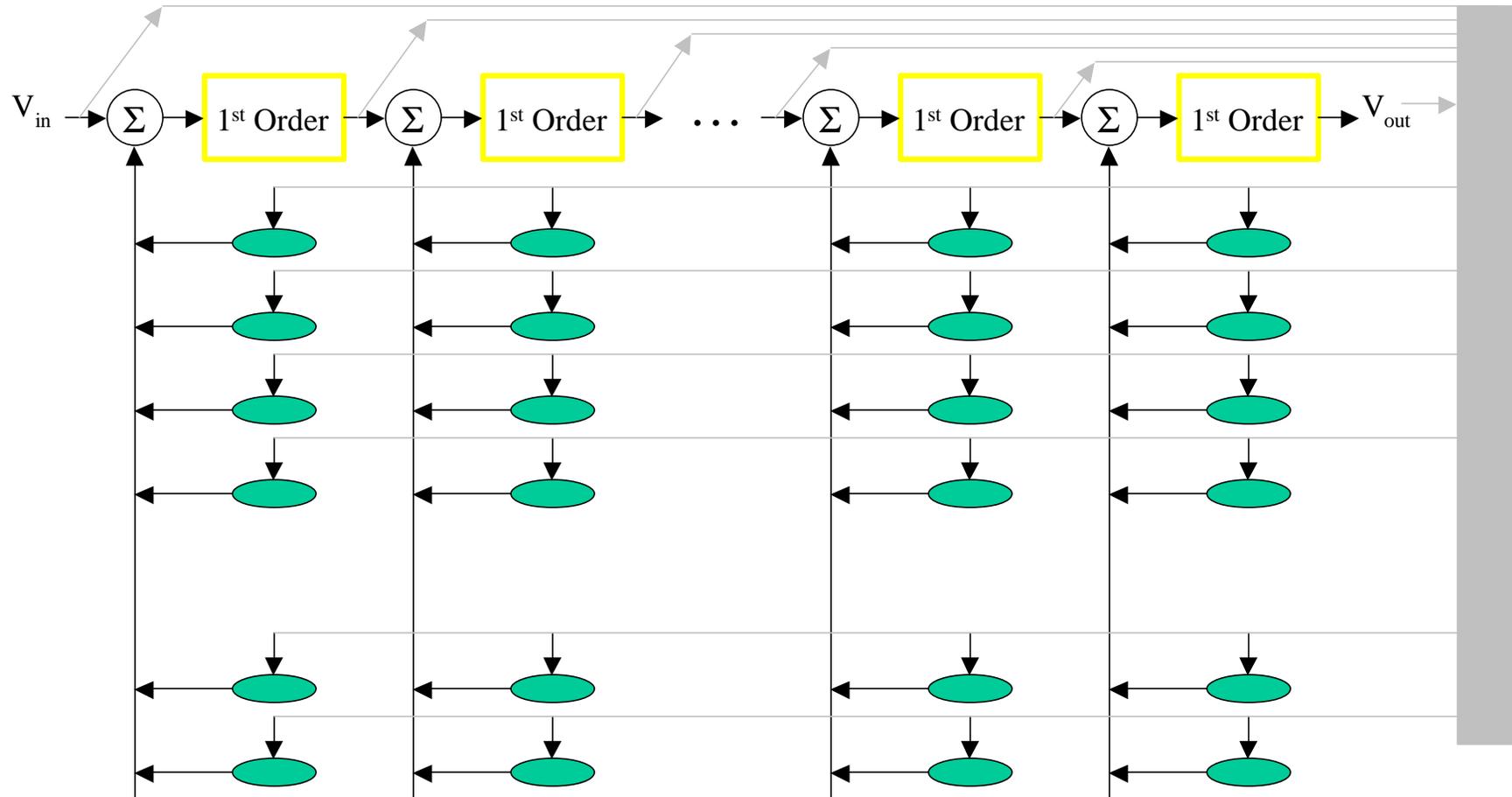

# General Filter Topology

$N*N$  parameters

$N$  poles,  $N$  zeros for  $N$ -th order filter

Problem is underspecified...therefore can optimize  
for SNR, complexity, etc...

# Partitioning $H(s)$ for Circuit Implementation


“Partition” the transfer function into simple parts

- Factorization into first order and second order terms
- Nearest neighbor feedback (~LC ladder filter network)
- Addition of factors  
(maybe out of an approximation of an FIR filter)
- Additional feedback / feedforward terms

Similar for either  $H(s)$  or  $H(z)$


# Typical Filter Topologies
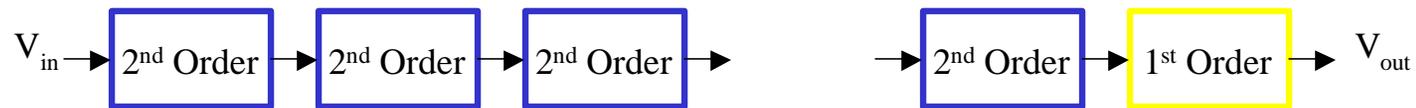
## Cascade of First and Second-Order Sections





# Typical Filter Topologies
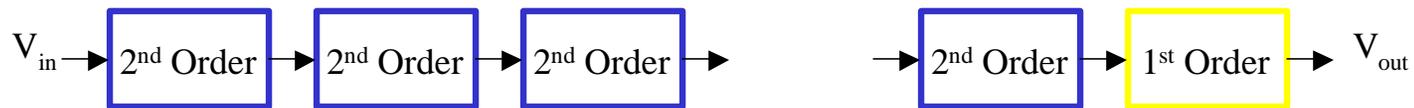
## Cascade of First and Second-Order Sections


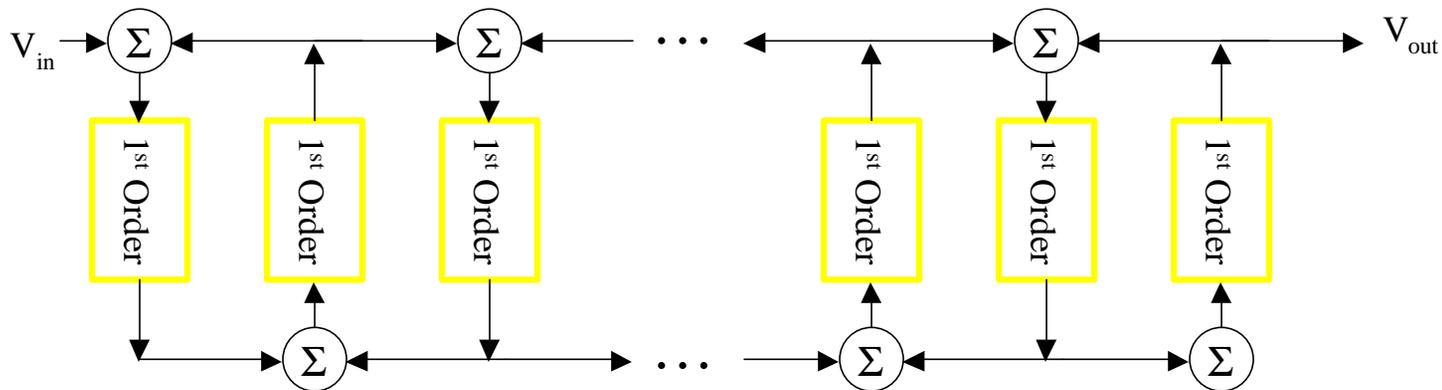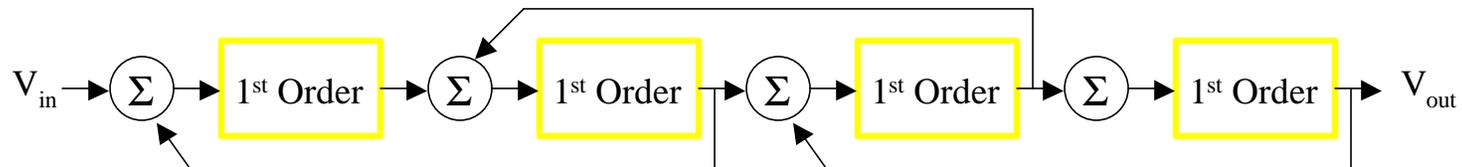
## Nearest Neighbor Feedback (Inspired by LC ladder network filters)



# Conclusions

Basic directions for integrated circuit filters

- Continuous or Discrete: Time and/or Amplitude
- High level specifications of filters
- Obtaining a filter function ( $H(s)$  or  $H(z)$ )
- Implementing the filter function into basic blocks  
(first and second-order filter sections, integrators, delays, etc.)